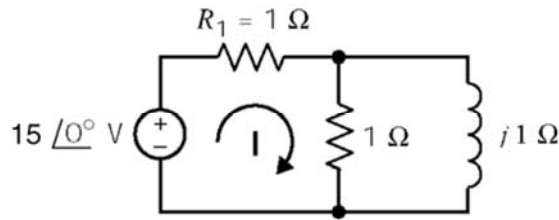


**P 11.3-8**

**Solution:**



The equivalent impedance of the parallel resistor and inductor is

$$\mathbf{Z} = \frac{(1)(j)}{1+j} = \frac{1}{2}(1+j) \Omega. \text{ Then}$$

$$\mathbf{I} = \frac{15\angle 0^\circ}{1 + \frac{1}{2}(1+j)} = \frac{30}{3+j} = \frac{30}{\sqrt{10}} \angle -18.4^\circ \text{ A}$$


$$(a) P_{\text{source}} = \frac{|\mathbf{I}||\mathbf{V}|}{2} \cos \theta = \frac{(15)\left(\frac{30}{\sqrt{10}}\right)}{2} \cos(-18.4^\circ) = 67.5 \text{ W}$$

$$(b) P_{R_1} = \frac{|\mathbf{I}|^2 R_1}{2} = \frac{\left(\frac{30}{\sqrt{10}}\right)^2 (1)}{2} = 45 \text{ W}$$

**P 11.5-3**

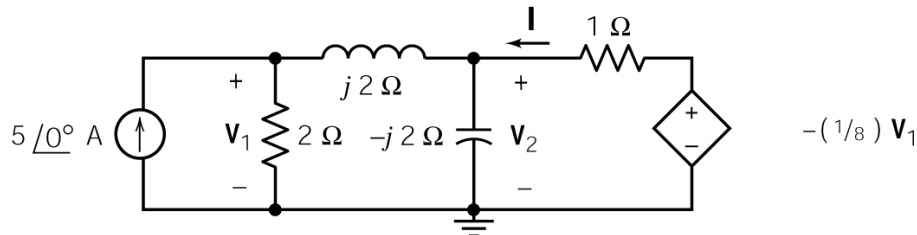**Solution:**

Represent the circuit in the frequency domain and label the node voltages:



The node equations are:

$$5\angle 0 = \frac{\mathbf{V}_1}{2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{j2} \Rightarrow \mathbf{V}_1(1-j) + j\mathbf{V}_2 = 10$$

$$\frac{\mathbf{V}_2 - \mathbf{V}_1}{j2} + \frac{\mathbf{V}_2}{-j2} + \frac{\mathbf{V}_2 - \left(-\frac{1}{8}\mathbf{V}_1\right)}{1} = 0 \Rightarrow \mathbf{V}_1(0.25+j) + \mathbf{V}_2(2) = 0$$

Using MATLAB:

$$\begin{bmatrix} 1-j & j \\ 0.25+j & 2 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \Rightarrow \mathbf{V}_1 = 5.33\angle 36.9^\circ \text{ V} \\ \mathbf{V}_2 = 2.75\angle -67.2^\circ \text{ V}$$

then

$$\mathbf{I} = \frac{-\frac{1}{8}\mathbf{V}_1 - \mathbf{V}_2}{1} = 2.66\angle 126.9^\circ \text{ A}$$

Now the complex power can be calculated as

$$\mathbf{S} = \frac{\mathbf{I}^* \left( -\left(\frac{1}{8}\right) \mathbf{V}_1 \right)}{2} = \frac{\left( 2.667 \angle 126.9^\circ \right)^* \left( -\frac{5.33}{8} \angle 36.9^\circ \right)}{2} = j0.8889 = j\frac{8}{9} \text{ VA}$$

Finally

$$\mathbf{S} = P + jQ = j\frac{8}{9} \Rightarrow P = 0, Q = \frac{8}{9} \text{ VAR}$$

(Checked using MATLAB and LNAP)

**P 11.6-10**

**Solution:**

$$(a) \mathbf{S} = \frac{(48 \angle 0^\circ)(1.076 \angle -8.3^\circ)^*}{2} = 25.82 \angle 8.3^\circ = 25.6 + j3.7 \text{ VA}$$

$$(b) \mathbf{V}_1 = \frac{2\mathbf{S}_1}{\mathbf{I}^*} = \frac{2(6.945 + j13.89)}{(1.076 \angle -8.3^\circ)^*} = \frac{2(15.53 \angle 63.4^\circ)}{(1.076 \angle 8.3^\circ)} = 28.87 \angle 55.1^\circ \text{ V}$$

$$\mathbf{Z}_1 = \frac{\mathbf{V}_1}{\mathbf{I}} = \frac{28.87 \angle 55.1^\circ}{1.076 \angle -8.3^\circ} = 26.83 \angle 63.4^\circ = 12 + j24 = 12 + j6(4) \Omega$$

$$R_1 = 12 \Omega \text{ and } L_1 = 4 \text{ H.}$$

$$(c) \theta = \cos^{-1}(0.56) = 56^\circ, |\mathbf{S}| = \frac{P}{pf} = \frac{4.63}{0.56} = 8.268 \text{ VA}$$

$$\mathbf{V}_3 = \frac{2(8.268 \angle 56^\circ)}{(1.076 \angle -8.3^\circ)^*} = 15.37 \angle 47.7^\circ \text{ V}$$

$$\mathbf{Z}_3 = \frac{\mathbf{V}_3}{\mathbf{I}} = \frac{15.37 \angle 47.7^\circ}{1.076 \angle -8.3^\circ} = 14.28 \angle 56^\circ = 8 + j11.83 = 8 + j6(1.97) \Omega$$

$$R_3 = 8 \Omega \text{ and } L_3 = 2 \text{ H.}$$

**P 11.8-3**

**Solution:**

$$\mathbf{Z}_t = 800 + j1600 \Omega \text{ and } \mathbf{Z}_L = \frac{R \left( \frac{-j}{\omega C} \right)}{R - \frac{j}{\omega C}} = \frac{R - j\omega R^2 C}{1 + (\omega RC)^2}$$


$$\mathbf{Z}_L = \mathbf{Z}_t^* \Rightarrow \frac{R \left( \frac{-j}{\omega C} \right)}{R - \frac{j}{\omega C}} = \frac{R - j\omega R^2 C}{1 + (\omega RC)^2} = 800 - j1600 \Omega$$

Equating the real parts gives

$$800 = \frac{R}{1 + (\omega RC)^2} = \frac{4000}{1 + [(5000)(4000)C]^2} \Rightarrow C = 0.1 \mu\text{F}$$

**P 11.9-8**

**Solution:**

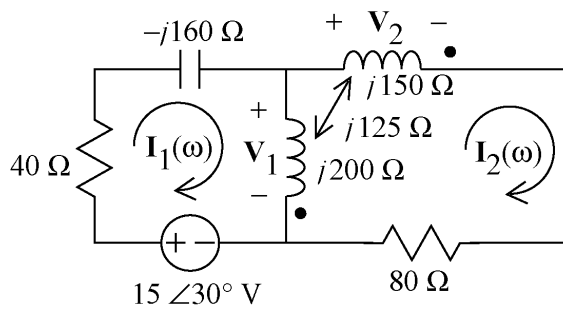

The equations describing the coupled coils give:

$$\begin{aligned} V_1 &= j200(I_1 - I_2) + j125 I_2 = j200 I_1 - j75 I_2 \\ V_2 &= j150 I_2 + j125(I_1 - I_2) = j125 I_1 + j25 I_2 \end{aligned}$$

The mesh equation for the left mesh is


$$\begin{aligned} -j160 I_1 + V_1 - 15 \angle 30^\circ + 40 I_1 &= 0 \\ -j160 I_1 + j200 I_1 - j75 I_2 - 15 \angle 30^\circ + 40 I_1 &= 0 \\ (40 + j40) I_1 - j75 I_2 &= 15 \angle 30^\circ \end{aligned}$$

The mesh equation for the right mesh is

$$\begin{aligned} V_2 + 80 I_2 - V_1 &= 0 \\ j125 I_1 + j25 I_2 + 80 I_2 - (j200 I_1 - j75 I_2) &= 0 \\ -j75 I_1 + (80 + j100) I_2 &= 0 \end{aligned}$$

**P 11.10-6**

**Solution:**

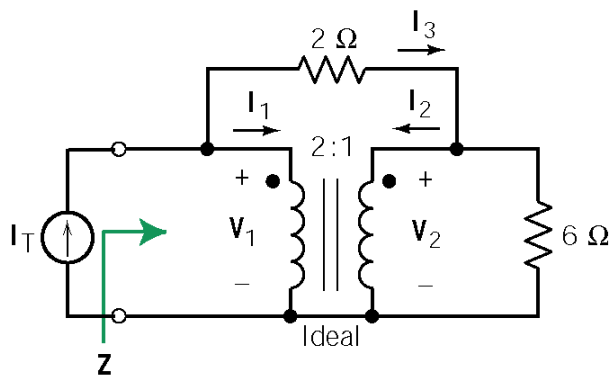

$$\begin{aligned} V_2 &= \frac{1}{2} V_1 \\ I_3 &= \frac{V_1 - V_2}{2} = \frac{V_1}{4} \\ I_2 &= I_3 - \frac{V_2}{6} = \frac{V_1}{6} \\ I_1 &= -\frac{1}{2} I_2 = -\frac{V_1}{12} \\ I_T &= I_3 + I_1 = \frac{V_1}{6} \\ Z &= \frac{V_1}{I_T} = 6 \end{aligned}$$