

P 13.2-18

Solution:

Represent the circuit in the frequency domain. Apply KCL at the inverting input node of the op amp to get


$$\frac{V_o - V_s}{R_1} + j\omega C_1 (V_o - V_s) - \frac{V_s}{R_2} = 0$$

or

$$(R_1 + R_2 + j\omega C_1 R_1 R_2) V_s = (R_2 + j\omega C_1 R_1 R_2) V_o$$

so
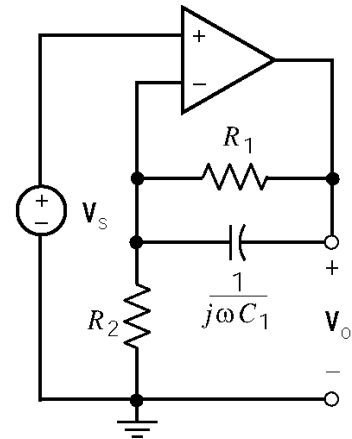
$$\mathbf{H} = \frac{V_o}{V_s} = \frac{R_1 + R_2 + j\omega C_1 R_1 R_2}{R_2 + j\omega C_1 R_1 R_2} = \frac{R_1 + R_2}{R_2} \times \frac{1 + j\omega C_1 \frac{R_1 R_2}{R_1 + R_2}}{1 + j\omega C_1 R_1}$$



With the given values


$$\mathbf{H} = \frac{V_o}{V_s} = \frac{7}{2} \frac{1 + \frac{j\omega}{7}}{1 + \frac{j\omega}{2}}$$

P 13.2-21

Solution:

Represent the circuit in the frequency domain. Apply KVL to the left mesh to get
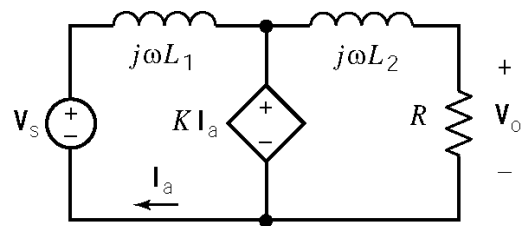
$$V_s = j\omega L_1 I_a + K I_a \Rightarrow I_a = \frac{V_s}{K + j\omega L_1}$$



Voltage division gives

$$V_o = \frac{R}{R + j\omega L_2} K I_a = \frac{R}{R + j\omega L_2} K \left(\frac{V_s}{K + j\omega L_1} \right) = \frac{R K}{(R + j\omega L_2)(K + j\omega L_1)} V_s$$

The network function of the circuit is

$$\mathbf{H} = \frac{\mathbf{V}_o}{\mathbf{V}_s} = \frac{1}{\left(1 + j\omega \frac{L_2}{R}\right) \left(1 + j\omega \frac{L_1}{K}\right)}$$

Comparing this network function to the specified network function gives


$$\frac{L_2}{R} = \frac{1}{30} \quad \text{and} \quad \frac{L_1}{K} = \frac{1}{60} \quad \text{or} \quad \frac{L_2}{R} = \frac{1}{60} \quad \text{and} \quad \frac{L_1}{K} = \frac{1}{30}$$

These equations do not have a unique solution. One solution is

$$L_1 = 0.07 \text{ H}, \quad L_2 = 0.16 \text{ H}, \quad R = 5 \Omega \text{ and } K = 2 \text{ V/A}$$

P 13.3-6

Solution:

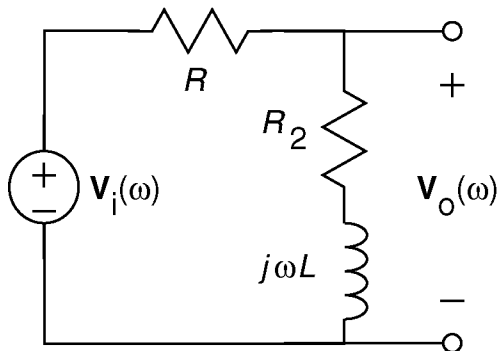

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_i(\omega)} = \frac{R_2 + j\omega L}{R + R_2 + j\omega L} \\ &= \left(\frac{R_2}{R + R_2} \right) \left(\frac{1 + j\omega \frac{L}{R_2}}{1 + j\omega \frac{L}{R + R_2}} \right) \end{aligned}$$

$$\mathbf{H}(\omega) = \frac{(0.2)(1 + j(0.2)\omega)}{1 + j(0.04)\omega} \Rightarrow \begin{cases} k = 0.2 \\ z = \frac{1}{0.2} = 5 \\ p = \frac{1}{0.04} = 25 \end{cases}$$

P 13.3-11


Solution:

$$\mathbf{H}(\omega) = -\frac{1}{R_1 \parallel \frac{1}{j\omega C_1}} = -\frac{1 + j\omega R_1 C_1}{j\omega R_1 C_2} = -\frac{1}{R_1 C_2} \frac{(1 + j\omega R_1 C_1)}{j\omega}$$

$$\mathbf{H}(\omega) \approx \begin{cases} -\frac{1}{R_1 C_2} \left(\frac{1}{j\omega} \right) & \omega < \frac{1}{R_1 C_1} \\ -\frac{1}{R_1 C_2} (R_1 C_1) = -\frac{C_1}{C_2} & \omega > \frac{1}{R_1 C_1} \end{cases}$$

With the given values:
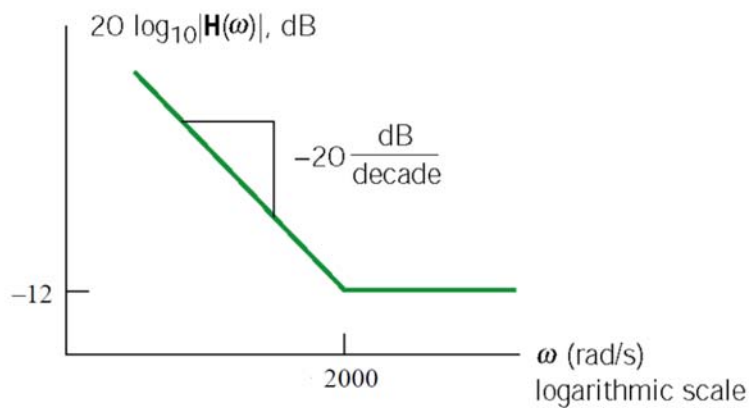
$$20 \log \left(\frac{C_1}{C_2} \right) = 20 \log(0.25) = -12 \text{ dB}, \quad \frac{1}{R_1 C_1} = 2000 \text{ rad/s}$$



P 13.4-2

Solution: For the parallel resonant RLC circuit we have

$$|\mathbf{H}(\omega)| = \frac{k}{\sqrt{1+Q^2 \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^2}}$$

so

$$R = k = |\mathbf{H}(\omega_0)| = \frac{8}{20 \cdot 10^{-3}} = 400 \, \Omega \quad \text{and} \quad \omega_0 = 1000 \text{ rad/s}$$

At $\omega = 897.6 \text{ rad/s}$, $|\mathbf{H}(\omega)| = \frac{4}{20 \cdot 10^{-3}} = 200$, so


$$200 = \frac{400}{\sqrt{1+Q^2 \left(\frac{897.6}{1000} - \frac{1000}{897.6} \right)^2}} \Rightarrow Q = 8$$

Then

$$\left. \begin{array}{l} \frac{1}{\sqrt{LC}} = \omega_0 = 1000 \\ 400\sqrt{\frac{C}{L}} = Q = 8 \end{array} \right\} \Rightarrow \begin{array}{l} C = 20 \mu\text{F} \\ L = 50 \text{ mH} \end{array}$$

P 13.6-1

Solution:

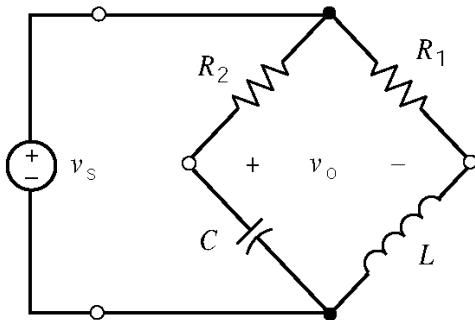

Using voltage division twice gives

$$\mathbf{V}_o(\omega) = \frac{\frac{1}{j\omega C}}{R_2 + \frac{1}{j\omega C}} \mathbf{V}_s(\omega) - \frac{j\omega L}{R_1 + j\omega L} \mathbf{V}_s(\omega)$$

so

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o(\omega)}{\mathbf{V}_s(\omega)} = \frac{1}{1 + j\omega C R_2} - \frac{j\omega L}{R_1 + j\omega L}$$

Modify the MATLAB script given in Section 13.7 of the text:

```
% P13_7_1.m - plot the gain and phase shift of a circuit

%-----
%   Create a list of logarithmically spaced frequencies.
%-----

wmin=1;      % starting frequency, rad/s
wmax=1000;   % ending frequency, rad/s

w = logspace(log10(wmin),log10(wmax));

%-----
%   Enter values of the parameters that describe the circuit.
%-----
```

```

R1 = 10; % Ohms
R2 = 20; % Ohms
C = 0.001; % Farads
L = 0.5; % Henries

%-----
% Calculate the value of the network function at each frequency.
% Calculate the magnitude and angle of the network function.
%-----

for k=1:length(w)
    H(k) = 1/(1+j*R2*C*w(k)) - j*L*w(k)/(R1+j*L*w(k));
    gain(k) = abs(H(k));
    phase(k) = angle(H(k))*180/pi;
end

%-----
% Plot the frequency response.
%-----

subplot(2,1,1), semilogx(w, gain)
xlabel('Frequency, rad/s'), ylabel('Gain, V/V')
title('Frequency Response Plots')
subplot(2,1,2), semilogx(w, phase)
xlabel('Frequency, rad/s'), ylabel('Phase, deg')

```

Here are the plots produced by MATLAB:

