

**P 14.4-1**  
**Solution**

$$F(s) = \frac{s+5}{s^3+3s^2+6s+4} = \frac{s+5}{(s+1)\left[(s+1)^2+3\right]} = \frac{A}{s+1} + \frac{Bs+C}{s^2+2s+4}$$

where

$$A = \left. \frac{s+5}{(s+1)^2+3} \right|_{s=-1} = \frac{4}{3}$$

Then

$$\frac{(s+5)}{(s+1)(s^2+2s+4)} = \frac{\frac{4}{3}}{s+1} + \frac{Bs+C}{s^2+2s+4} \Rightarrow (s+5) = \left(\frac{4}{3} + B\right)s^2 + \left(\frac{8}{3} + B + C\right)s + \frac{16}{3} + C$$

Equating coefficient yields

$$s^2: 0 = \frac{4}{3} + B \Rightarrow B = -\frac{4}{3}$$

$$s: 1 = \frac{8}{3} - \frac{4}{3} + C \Rightarrow C = -\frac{1}{3}$$

Then

$$F(s) = \frac{\frac{4}{3}}{s+1} + \frac{-\frac{4}{3}s + \frac{1}{3}}{(s+1)^2+3} = \frac{\frac{4}{3}}{s+1} + \frac{-\frac{4}{3}(s+1)}{(s+1)^2+3} + \frac{\frac{1}{\sqrt{3}}\sqrt{3}}{(s+1)^2+3}$$


Taking the inverse Laplace transform yields

$$f(t) = \frac{4}{3}e^{-t} - \frac{4}{3}e^{-t} \cos \sqrt{3}t + \frac{1}{\sqrt{3}}e^{-t} \sin \sqrt{3}t$$

**P14.6-1**

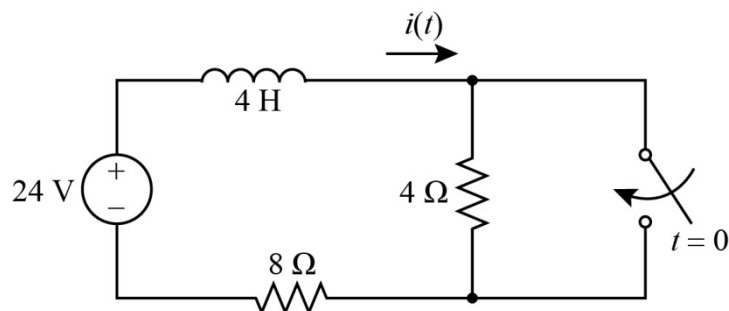**Solution:**

In order to find the inductor current  $i(t)$  proceed as follows:



When the switch is closed for the circuit shown in the figure above, the Kirchhoff's Voltage Law (KVL) is applied to obtain the inductor current  $i(t)$  as follows:

$$-24 + 4 \frac{di(t)}{dt} + 8i(t) = 0$$

$$i(0) = \frac{24}{4+8} = 2$$

---

Apply Laplace Transform:

$$4sI(s) - 4i(0) + 8I(s) = \frac{24}{s}$$

$$I(s)[4s+8] = \frac{24}{s} + 8$$

$$i(s) = -\frac{24}{s(4s+8)} + \frac{8}{4s+8}$$

$$= \frac{6}{s(s+2)} + \frac{2}{s+2} = \frac{3}{s} - \frac{3}{s+2} + \frac{2}{s+2} = \frac{3}{s} - \frac{1}{s+2}$$

---

Now apply the Inverse Laplace transform to obtain  $i(t)$  as follows:


$$\begin{aligned} i(t) &= 3 - 3e^{-2t} + 2e^{-2t} \\ &= 3 - e^{-2t} \end{aligned}$$

Hence, inductor current  $i(t)$  is  $\boxed{3 - e^{-2t}}$

**P 14.7-14** Determine the current  $i_L(t)$  for  $t \geq 0$  for the circuit of Figure P 14.7-14.

**Hint:**  $v_C(0) = 8 \text{ V}$  and  $i_L(0) = 1 \text{ A}$


**Answer:**  $i_L(t) = \left( e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t \right) u(t) \text{ A}$

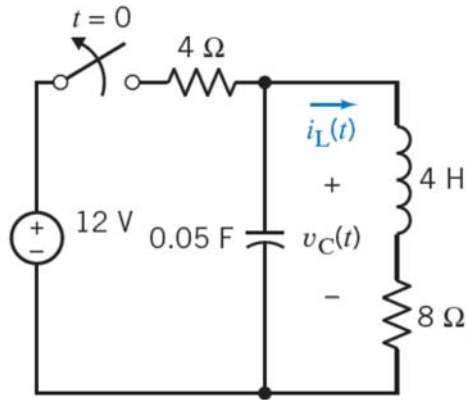

**Figure P 14.7-14**

**P 14.7-14**

**Solution:**

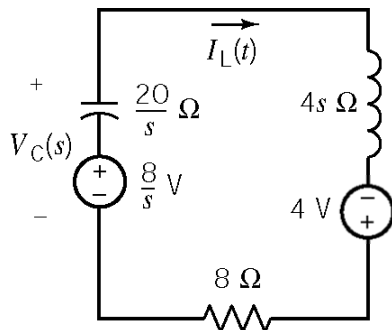

KVL:

$$\frac{8}{s} + 4 = \left( \frac{20}{s} + 8 + 4s \right) I_L(s)$$

so

$$I_L(s) = \frac{2+s}{s^2+2s+5} = \frac{(s+1)+1}{(s+1)^2+4}$$

Taking the inverse Laplace transform:

$$i_L(t) = \left( e^{-t} \cos 2t + \frac{1}{2} e^{-t} \sin 2t \right) u(t) \text{ A}$$


**P14.8-7**

**Solution:** First, determine the transfer function from the circuit. To do so, represent the circuit in the  $s$ -domain as shown.

Recognizing the noninverting amplifier we

$$V_a(s) = \left( 1 + \frac{\frac{10^7}{s} \parallel 10^4}{10^4} \right) V_i(s) = \left( 1 + \frac{\frac{10^7}{s+10^3}}{10^4} \right) V_i(s)$$
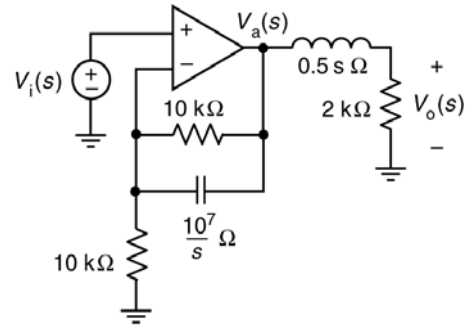
$$= \left( \frac{s+2000}{s+1000} \right) V_i(s)$$



(Alternately, this equation can be obtained by applying KCL at the inverting input node of the op amp.)

Use voltage division to write

$$V_o(s) = \frac{2000}{2000 + 0.5s} V_a(s) = \frac{4000}{s + 2000} V_a(s)$$

The transfer function is

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{4000(s+2000)}{(s+1000)(s+4000)}$$


The step response is

$$v_o(t) = \mathcal{L}^{-1} \left[ \frac{H(s)}{s} \right] = \mathcal{L}^{-1} \left[ \frac{4000(s+2000)}{s(s+1000)(s+4000)} \right] = \mathcal{L}^{-1} \left[ \frac{2}{s} + \frac{-4/3}{s+1000} + \frac{-2/3}{s+4000} \right]$$

$$v_o(t) = \left[ 2 - \left( \frac{4}{3} e^{-1000t} + \frac{2}{3} e^{-4000t} \right) \right] u(t) \text{ V}$$

**P 14.8-9**

**Solution:**

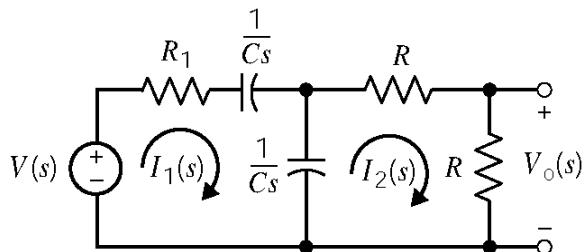

Mesh equations:

$$V(s) = \left( R_1 + \frac{1}{Cs} + \frac{1}{Cs} \right) I_1(s) - \frac{1}{Cs} I_2(s)$$

$$0 = \left( R + R + \frac{1}{Cs} \right) I_2(s) - \frac{1}{Cs} I_1(s)$$

Solving for  $I_2(s)$ :

$$I_2(s) = \frac{V(s) \left( \frac{1}{Cs} \right)}{\left( R_1 + \frac{2}{Cs} \right) \left( 2R + \frac{1}{Cs} \right) - \frac{1}{(Cs)^2}}$$

Then  $V_o(s) = RI_2(s)$  gives

$$H(s) = \frac{V_o(s)}{V(s)} = \frac{RCs}{[R_1Cs+2][2RCs+1]-1} = \frac{s}{2R_1C \left[ s^2 + \frac{4RC+R_1C}{2RR_1C^2}s + \frac{1}{(2RR_1C^2)^2} \right]}$$


### P14.9-1

#### Solution:

To solve this problem using convolution, we first represent the input is by the function

$$v_i(t) = \begin{cases} 0 & t \leq 2 \\ 10t - 20 & 2 \leq t \leq 3 \\ -7.5t + 32.5 & 3 \leq t \leq 5 \\ 5t - 30 & 5 \leq t \leq 6 \\ 0 & 6 \leq t \end{cases}$$

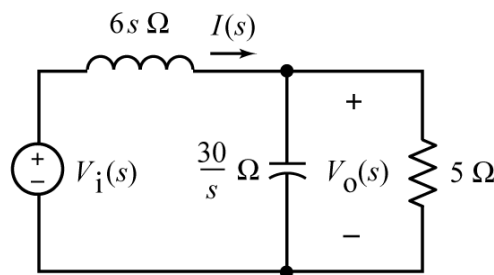Next, we obtain the impulse response. To do so, assume that the initial conditions are zero and represent the circuit in the s-domain as



Using voltage division and equivalent impedance, the transfer function is

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{\frac{30}{s} \parallel 5}{6s + \frac{30}{s} \parallel 5} = \frac{\frac{30}{s+6}}{6s + \frac{30}{s+6}} = \frac{5}{s^2 + 6s + 5} = \frac{1.25}{s+1} - \frac{1.25}{s+5}$$

The impulse response is

$$h(t) = \mathcal{L}^{-1}[H(s)] = \mathcal{L}^{-1} \left[ \frac{1.25}{s+1} - \frac{1.25}{s+5} \right] = (1.25e^{-t} - 1.25e^{-5t})u(t)$$

Edit the MATLAB script from Example 14.9.1 to obtain

```
% P14_9_1.m - plots the output for Problem
14.9-1
% -----
% Obtain a list of equally spaced instants of
time
% -----
t0 = 0; % begin
tf = 12; % end
N = 5000; % number of points plotted
dt = (tf-t0)/N; % increment
t = t0:dt:tf; % time in seconds

% -----
% Obtain the input x(t) and the impulse
response h(t)
% -----
for k = 1 : length(t)
    if t(k) < 2
        x(k) = 0;
    elseif t(k) < 3
        x(k) = -20 + 10*t(k); %
    elseif t(k) < 5
        x(k) = +32.5 - 7.5*t(k); %
    elseif t(k) < 6
        x(k) = -30 + 5*t(k); %
    else
        x(k) = 0;
    end
end
x=x*dt;
h=1.25*exp(-t)-1.25*exp(-5*t);

% -----
% Perform the convolution
% -----
y=conv(x,h);

% -----
% Plot the output y(t)
% -----
plot(t,y(1:length(t)))
axis([t0, tf, -5, 10])
xlabel('t')
ylabel('y(t)')
```

Running this script produces the required plot of the output voltage:

