

---

# Introduction to Electric Circuits

Review


# Linear Time-invariant Circuits

---


- Linear function, Nonlinear function

$$f(x_1 + x_2) = f(x_1) + f(x_2)$$


$$f(Kx) = Kf(x)$$

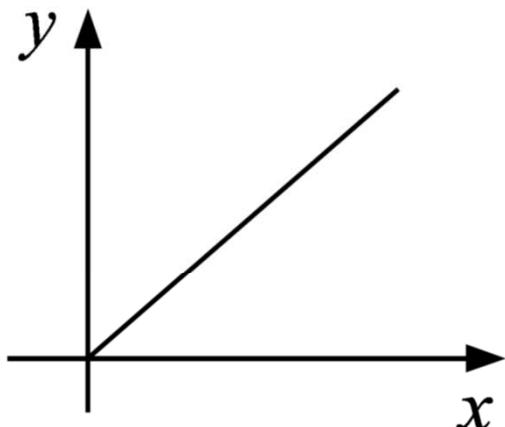

$$y = f(x) = Kx$$

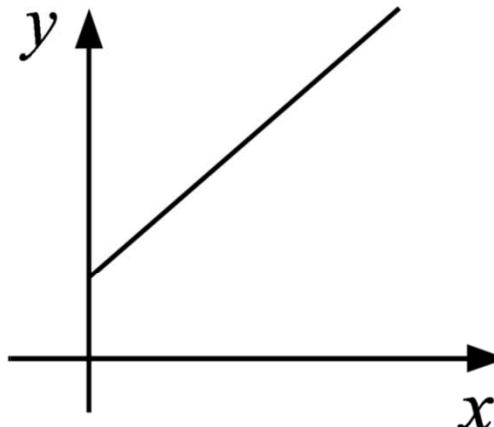



$$y = f(x) = Kx + b$$

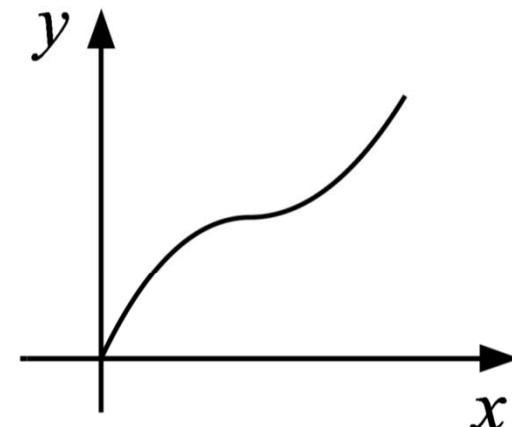

$$y = f(x)$$




# Linear Resistor

---

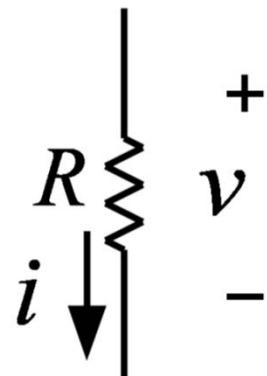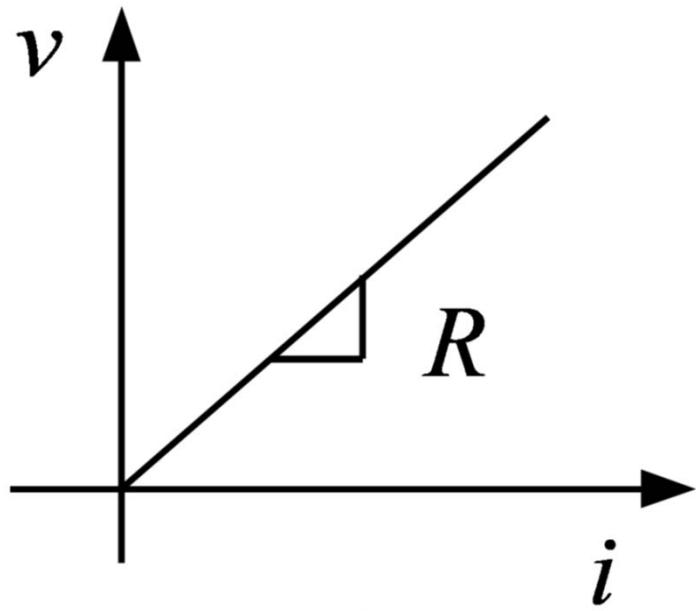

# Linear Capacitor

---

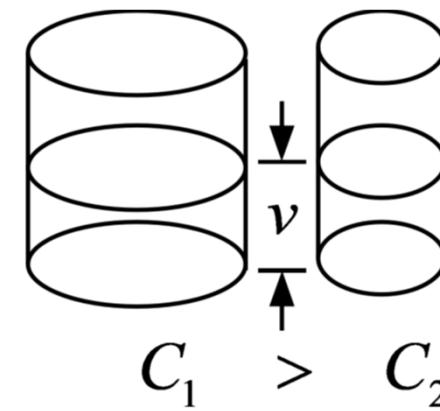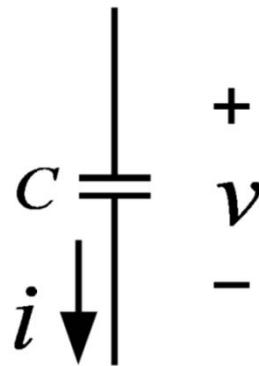
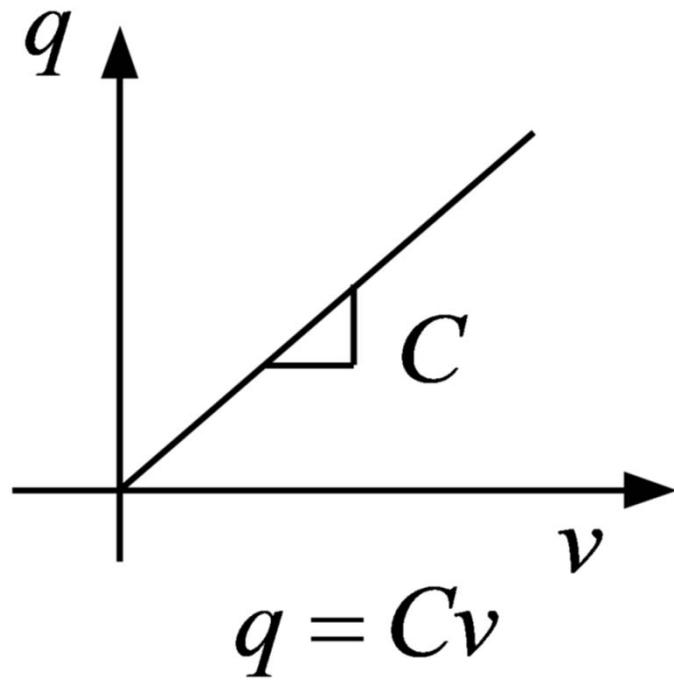


$$q_1 = C_1 v \quad > \quad q_2 = C_2 v$$

$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$



# Linear Inductor

---

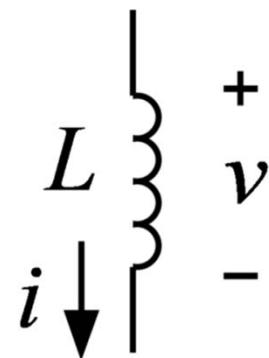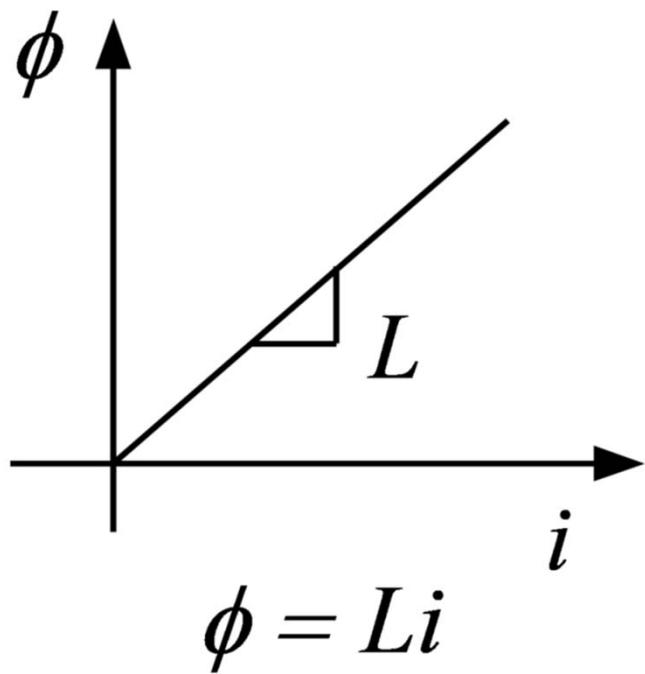

$$v = \frac{d\phi}{dt} = L \frac{di}{dt}$$

# RC Circuit

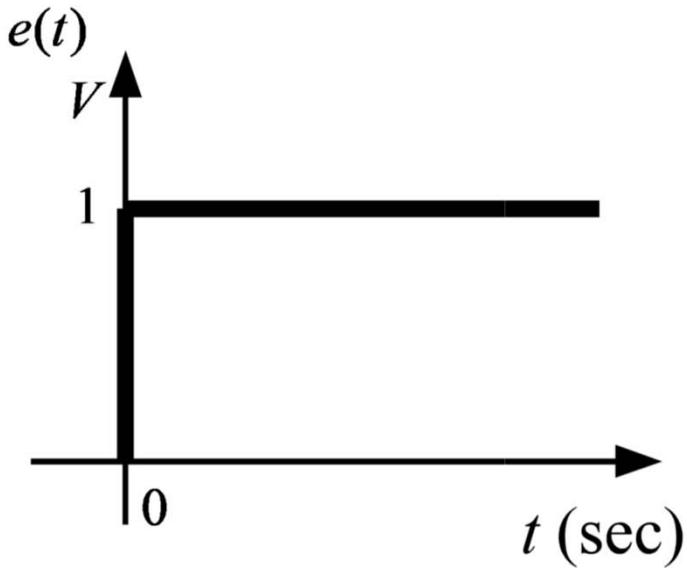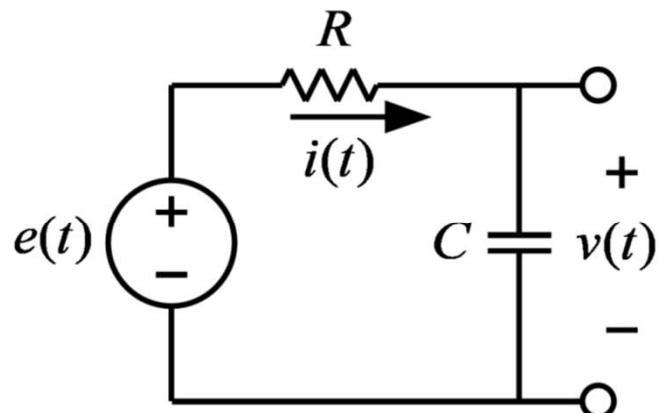

*KVL:*

$$Ri + v = e, \quad i = C \frac{dv}{dt}$$

$$RC \frac{dv}{dt} + v = e, \quad v(0) = 0$$

- 
- Complete response = natural response + forced response
  - Natural response(homogeneous solution):

$$RC \frac{dv}{dt} + v = 0$$

$$RCs + 1 = 0 \Rightarrow s = -\frac{1}{RC}$$

$$v(t) = Ke^{-\frac{t}{RC}}$$

- Forced response(particular solution), steady state:

$$v = V_{ss}$$


$$RC \frac{dV_{ss}}{dt} + V_{ss} = 1 \Rightarrow V_{ss} = 1$$



- 
- Complete response = natural response + forced response

$$v(t) = Ke^{-\frac{t}{RC}} + 1$$

$$v(0) = K + 1 = 0 \Rightarrow K = -1$$

$$v(t) = -e^{-\frac{t}{RC}} + 1$$

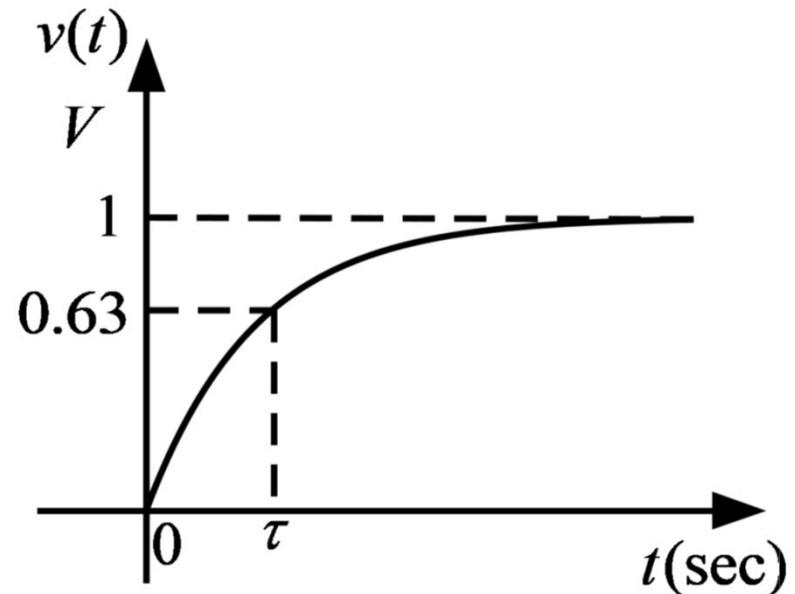

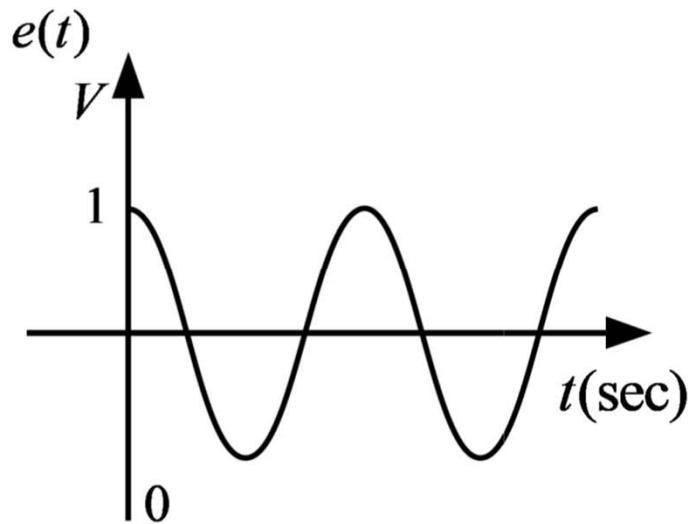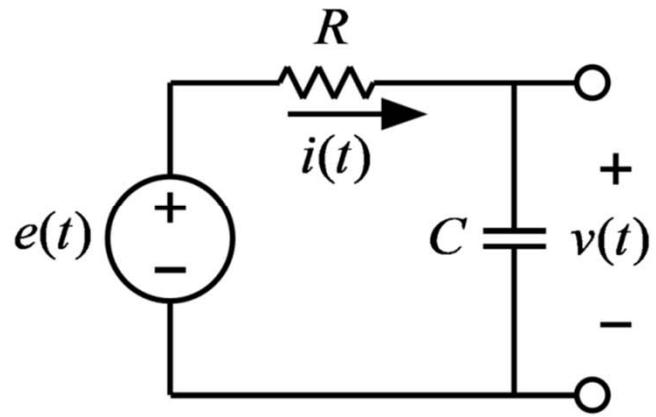

*KVL :*

$$Ri + v = e = \cos \omega t, \quad i = C \frac{dv}{dt}$$

$$RC \frac{dv}{dt} + v = \cos \omega t, \quad v(0) = 1$$

- 
- Forced response(particular solution), steady state:

$$v = A \cos \omega t + B \sin \omega t$$

$$RC \frac{d(A \cos \omega t + B \sin \omega t)}{dt} + (A \cos \omega t + B \sin \omega t) = \cos \omega t$$

$$-\omega R C A \sin \omega t + \omega R C B \cos \omega t + A \cos \omega t + B \sin \omega t = \cos \omega t$$

$$(\omega R C B + A) \cos \omega t + (B - \omega R C A) \sin \omega t = \cos \omega t$$

$$\omega R C B + A = 1, B - \omega R C A = 0$$

$$B = \omega R C A, \omega R C (\omega R C A) + A = 1$$

$$A = \frac{1}{(\omega R C)^2 + 1}, B = \frac{\omega R C}{(\omega R C)^2 + 1}$$

- 
- Forced response(particular solution), steady state:

$$\begin{aligned}v &= A \cos \omega t + B \sin \omega t \\&= \frac{1}{(\omega RC)^2 + 1} \cos \omega t + \frac{\omega RC}{(\omega RC)^2 + 1} \sin \omega t \\&= \frac{\sqrt{(\omega RC)^2 + 1}}{(\omega RC)^2 + 1} \cos(\omega t - \tan^{-1} \omega RC) \\&= \frac{1}{\sqrt{(\omega RC)^2 + 1}} \cos(\omega t - \tan^{-1} \omega RC)\end{aligned}$$

---

- Complete response

$$v(t) = Ke^{-\frac{t}{RC}} + \frac{1}{(\omega RC)^2 + 1} \cos \omega t + \frac{\omega RC}{(\omega RC)^2 + 1} \sin \omega t$$

$$= Ke^{-\frac{t}{RC}} + \frac{1}{\sqrt{(\omega RC)^2 + 1}} \cos(\omega t - \tan^{-1} \omega RC)$$

$$v(0) = K + \frac{1}{(\omega RC)^2 + 1} = 1, K = \frac{(\omega RC)^2}{(\omega RC)^2 + 1}$$

$$v(t) = \frac{(\omega RC)^2}{(\omega RC)^2 + 1} e^{-\frac{t}{RC}} + \frac{1}{(\omega RC)^2 + 1} \cos \omega t + \frac{\omega RC}{(\omega RC)^2 + 1} \sin \omega t$$

---

- Check

$$v(t) = \frac{(\omega RC)^2}{(\omega RC)^2 + 1} e^{-\frac{t}{RC}} + \frac{1}{(\omega RC)^2 + 1} \cos \omega t + \frac{\omega RC}{(\omega RC)^2 + 1} \sin \omega t$$

$$\frac{dv(t)}{dt} = -\frac{1}{RC} \frac{(\omega RC)^2}{(\omega RC)^2 + 1} e^{-\frac{t}{RC}} - \frac{\omega}{(\omega RC)^2 + 1} \sin \omega t + \frac{\omega^2 RC}{(RC\omega)^2 + 1} \cos \omega t$$

$$\left. \frac{dv(t)}{dt} \right|_{t=0} = -\frac{1}{RC} \frac{(\omega RC)^2}{(\omega RC)^2 + 1} + \frac{\omega^2 RC}{(\omega RC)^2 + 1} = 0$$